Tio TK-701S Ex-PMR Genversion

Dave Comber G8UYZ shows how to get the Trio TK-701S VHF ex-PMR transceiver going on 2m in this follow-up article to the HRT TK-801S conversion

The VHF 'sister set' to the Trio TK-801S UHF mobile (featured in the May 94 issue of HRT) is the TK-701S, hich can be modified to run on 2m. here is also rumoured to be a TK-501S on about 4m, but these have not often been seen in the UK and response to a WWW on packet radio has yet to indicate anything different anywhere else.

The conversion requires the careful installation of extra ceramic capacitors (size = 2.54 pitch), on parts of the TX/RX board. It may also be possible to change the existing capacitors, replacing with the correspondingly higher value. Board construction (and your skills), may make this a bit difficult. Tuning up is basically the same procedure as for the TK-801S, it is important you have the toning details of the 801S to hand.

Before converting your rig, make sure the set is working and that the IFs and discriminators are aligned as they should be if the set has come out of service. If this is not the case, align or repair the set on its existing frequencies before carrying out any modifications.

Ranoving the H. Khoard

This is not an easy board to remove (there are several active devices bolted to the chassis, which

also forms part of the heat sink). You should have a multi-section box in which to keep all the screws (they are not all the same).

Remove the front panel, complete, then remove the diecast cover from the TX/RX board (watch where there are long screws). Remove the screws in the PCB and the ones retaining the active dev ces; IC U17, U16, Q3, Q4 and Q6. Double check these as it is very easy to break something! Remove the screws retaining the aerial outrut socket, then unsolder and remove the aerial connector (keep these!). Disconnect J21 and J22. Lift the board out, keeping it straight up for at least 12mm before moving forward, as there are multiple connectors connecting to the PLL beard. See the components list for details of component changes.

The IVI XIV and AUX switches

Now is a good time to look at the connections to the MON switch.
Remove C 25 (between the switches).
Ensure that JU2001 is open circuit.
Cut the earth track on the centre contact of the inside change-over so:
(you can use it to switch the earth on the repeater LEDs, in which case, check that it is a good solid earth connection, it may require an extra wire).

Re-fitting the PCB

The control of the

Contract Contract Contract

i de la régi**o**s Souscios

1.88981

When re-fitting the board, make sure that the connectors are in alignment. The board should be a good fit to the diecast case before you do any screwing down!

Warning: PA transistors are not cheap (some of the ICs are tricky to get as well). Don't forget to re-fit the aerial connector (you can fit either an 'N' type or an SO239, both will fit the chassis). If the board has gone in smoothly, re-fit all the screws. You may now think about doing the tuning up.

Tune-up procedure

The PLL is set up the same way as for the TK-801S, with the following exception: TX PLL C903 should be adjusted for the lowest voltage consistent, with operation at both ends of the band, i.e. about 3 - 3.5V (you might get it down to 2.5V, but it may depend upon how good you are at installing the extra components!). The RX PLL is exactly the same.

nochar alignment

gadalika babil

The trib and requirements are sexectly use same procedure; set for a channel in the middle of the band.

Tune for maximum received signal strength, tuning in the following order; L20, L21, L23, L24, L25, L18, L19. Reduce the signal generator input and repeat, several times, until no further improvement can be heard. Adjust L30 for best signal to noise figure.

This bit is only needed if the AF response leaves a bit to be desired; adjust L32 for maximum AF output, L29 and L26 for minimum distortion, in that order. You should get better than 0.5µV for 17dB (0.2µV is not impossible). The squelch threshold is adjusted the same way as for the TK-801S.


Transmitter alignment

ATTO NOTES A

14 13 F

Asherit

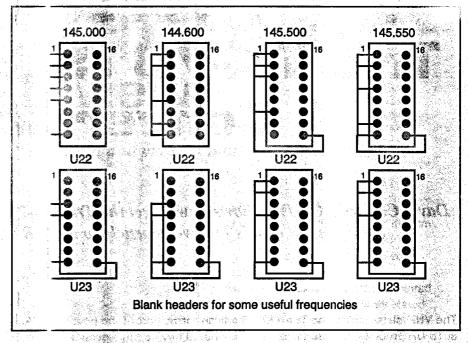
I assume that the radio worked before you started modifying it! You will need the same equipment as for the TK-801S, but the tuning tool is



hexagonal.

Connect the PSU, ammeter (if external), the dummy load/\(\sigma\) /attmeter and the microphone. Set R\(\sigma\)301 fully clockwise before

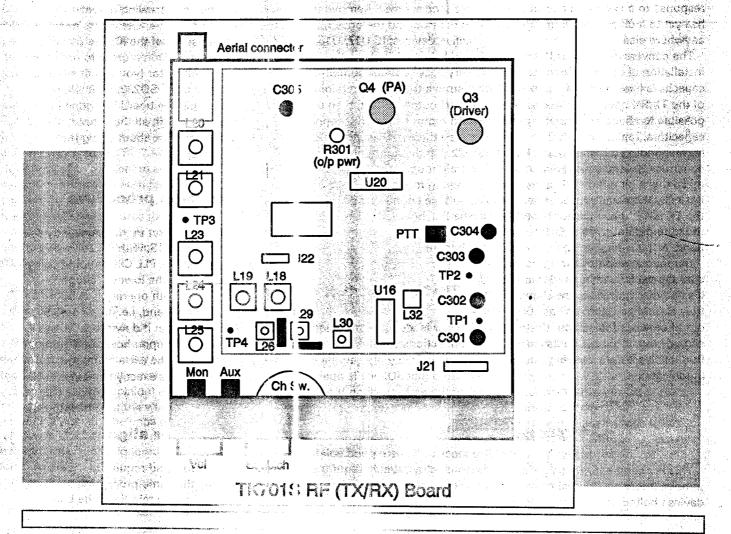continuing. Tune the following, in this order; C301, C302, C303, C304 and C305 for maximum RF output. Repeat several times, finally tuning for the 'dip' in consumed current



1999

Some useful char	noi codes		
Ch Freg. N	Binary N	A	Binary A
28 144.5000 461	1011001110	40	000101
2A 144.5250 461 2C 144.5500 461	1011001110 1011001110	46 52	011101 *** 001011 ***
2E 144.5750 461	· · · · · · · · · · · · · · · · · · ·	58	0.0111
30 144.6000 462	1. 加入的機能性 (A)	0	000000
31 144.6125 462 32 144.6250 462		3 6	1 0000 \$
33 144.6375 462	· · · · · · · · · · · · · · · · · · ·	9 7	100100
34 144.6500 462		12	001100
35 144.6625 462 36 144.6750 462	1 4 4 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5	15 18	111100 010010
37 144.6875 462		21 🗽	101010
38 144.7000 462	大学教 · 法是第一条 · · · · · · · · · · · · · · · · · · ·	24	0(10110
50 145.000 463 52 145.025 463		32 38	0(·0001)
54 145.050 463	A CONTRACT OF THE PARTY OF THE	44	001101
56 145.07 5 463		50	010011
58 145.100 463 5A 145.125 463	the second secon	56 61	000111
5C 145.150 464	A Marie La Grand Land	4	001000
5E 145.175 464	Company of the Compan	10	010100
60 145.200 464 62 145.225 464	3343.43.4	16 22	000010a
64 145,250 3 464	1.45/51.15.45	28	001110
66 145.275 464	Compare affects.	34	010001
68 145.300 464 6A 145.325 464	1.15 51	40 46	000 101
6C 145.350 464	CHE FIRE	52	001011
6D 145.3625 464	CANAL CONTRACTOR	55	111011
6E 145.375 464 6F 145.3875 464	0000101110	58	010111 **** 0(1111 ***
70 145.4 485	· 机类型线性	0	0(0000
71 145.4125 465	1000101110	3	110000
72 145.425 465 73 145.4375 465	1000101110 1000101110	6 9	011000 100100
74 145.45 465	1000101110	12	0(1100
75 145.4625 465	1000101110	15	111100 🎢
76 145.475 465 77 145.4875 465	1000101110 1000101110	18 21	010010 / 101010
77 145.4675 465 78 145.5 465	10 2 W	24	0(0110
79 145.5125 465	7 4 4414	27	110 110
	1000101110 1000101110	30 33	01110 - 100001
and the second s	1000101110	36	001001
7D 145.5625 465	(1) (1) (1) (1) (1) (1) (1) (1) (1) (1)	39	1 1001
7E 145.575 465 7F 145.5875 465	1000101110 1000101110	42 45	0 0101 101101
	1000101110	48	000011
	1000101110	51	1 0011
82 145.625 465 83 145.6375 465	1000101110 1000101110	54 57	0: 1011 % 100111
84 145.65 465	· 傳統的經濟學	59	1 0111
5a.	1000101110	62	0 1111
	0100101110	2 5	0 0000 101000
5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5	0100101110	8	000100
89 145.7125 466	0100101110	11	1 0100
8A 145.725 466 8B 145.7375 466	0100101110 6100101110	14 17	0 1100 100010
	েকুট 0100101110	20	001010
	0100101110	23	1 1010
8E 145.775/ 1468 8F 145.7875 466		26 29	0 0110 101110
90 145.8 466	0100101110	32	000001
10-07 70 1-17 時間 線(対)			1.1 9

commensurate with maximum RF output power (50W out, about 10A consumption, they get greedy and hot at 60W out!).

Reduce RV301 fully anti-clockwise and adjust C303, C304 and C305 only for the maximum output RF power, tuning for the 'dip' in consumed current commensurate with the required RF output power. It should be possible to adjust between 15W and 55W output, using RV301. I found that 25W is ideal for most operations, including packet radio. Note that the duty cycle is rated at 20% for transmit on full output, so reducing and careful tuning will improve this figure. Tune L15 for the exact required transmit frequency.

Adjust RV901 for correct deviation and RV902 for an appropriate microphone gain (usually well up).

EPROM conversion

C29

C30, 40, 43

lead lengths.

1

The EPROM conversion to these sets is exactly the cases same as the TK-801 (although the data in the EPROMs term is of course different). If you'd like a ready-made source of EPROMs for the TK-701, contact Kev Graham and G8ZWU, 670 Stafford Rd., Fordhouses, Wolverhampton WV10 6NW for details, please don't extract forget to enclose a stamped addressed envelope for the case reply.

asilka arrebi

173.7 000 1 1.46.70 31

vertical, it isolates

plenu con anze c

mocara nabilitar

> > . N ciret

esti.

+18p 🖟 🖼

+4p7

If you have any queries on this conversion 'follow up', you may contact the author, enclosing an SAE for clear reply, to; Dave Coomber G8UYZ, 14 Francis Green Ln., not Penkridge, Staffs ST19 5HF.

Capacitor Additions	
Required;	
	그 사람이 가는 사람이 되었다.
Receiver	
	TOR. 7. F
C61, 63, 65, 69, 76, 80, 83	+2p2
- C38, 41	+10p 🛍 🗀 🗀
C40, 43	+4p7 ≫ 🎉
C42	+5p6 🚌 🤾 🕻
Note; the above should all be	fitted directly, 🐠 🙃
underneath the PCB, with the s	hortest possible leads,
and should be soldered to lie fl	
Transmitter	
C6, 20, 38, 41	+10p 🖖 🚶
C12	
C18, 42	
C23, 24, 28	+33p


Note; The above may all be soldered on the side of component side, across existing components mounted vertically, again use the shortest possible of

FIT EXTRA CAPACITORS IN POSITIONS SHOWN

KENWOOD GENUINE PARTS NOTE REVISED VALUES FOR CZ4/C

TK-701S Final TR Q4.....2SC2630

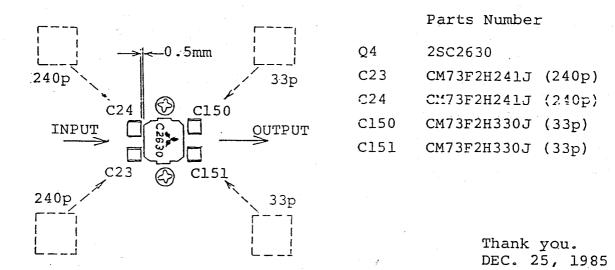Note 1. Automatically raplace these chip capacitors when removing or replacing this transistor. (Follow the picture)



TRIO-KENWOOD CORPORATION TOKYO